

BANDPASS FILTER DESIGN IN SIMULINK:

Step 1: We design the basic RLC circuit of a bandpass filter by following the below schematic and putting the values of RLC as:

CONSTANTS:

$$R = 1000 \, \Omega$$

$$L = 27 \, \text{mH}$$


$$C = 0.047 \, \mu\text{F}$$

$$\text{AC Voltage Peak Amplitude} = 10 \, \text{V}$$

VARIABLES:

AC Voltage Frequency

SCHEMATIC:

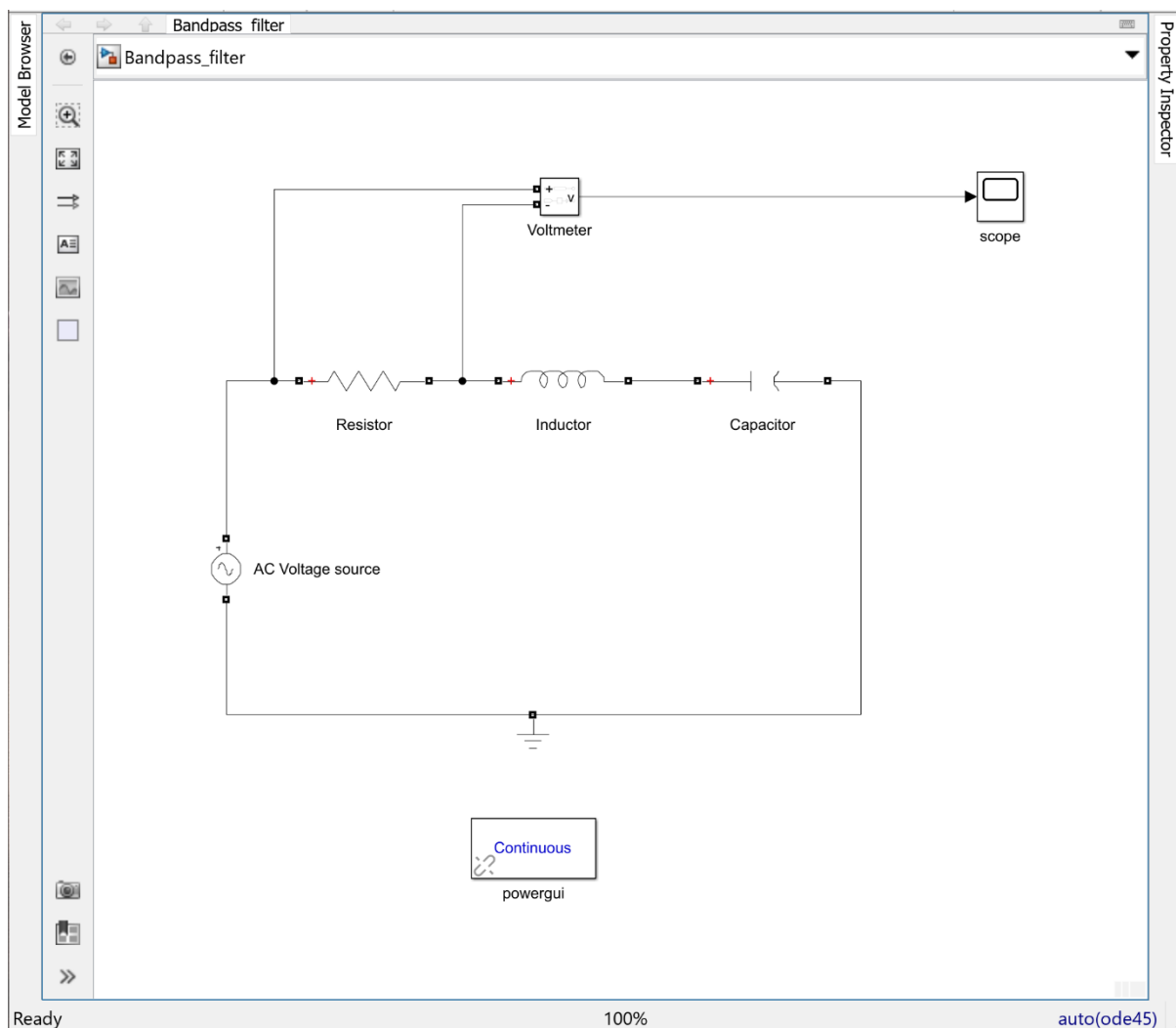

NOTE: Make sure you have 'Simscape Electrical Library' installed as an Add-On in Simulink

CALCULATION OF RESONANT FREQUENCY IN MATLAB:

```
Command Window
>> L=0.027

L =

    0.0270

>> C=0.047*10^-6

C =

    4.7000e-08


>> f=1/(2*pi*sqrt(L*C))

f =

    4.4678e+03

fx>> |
```

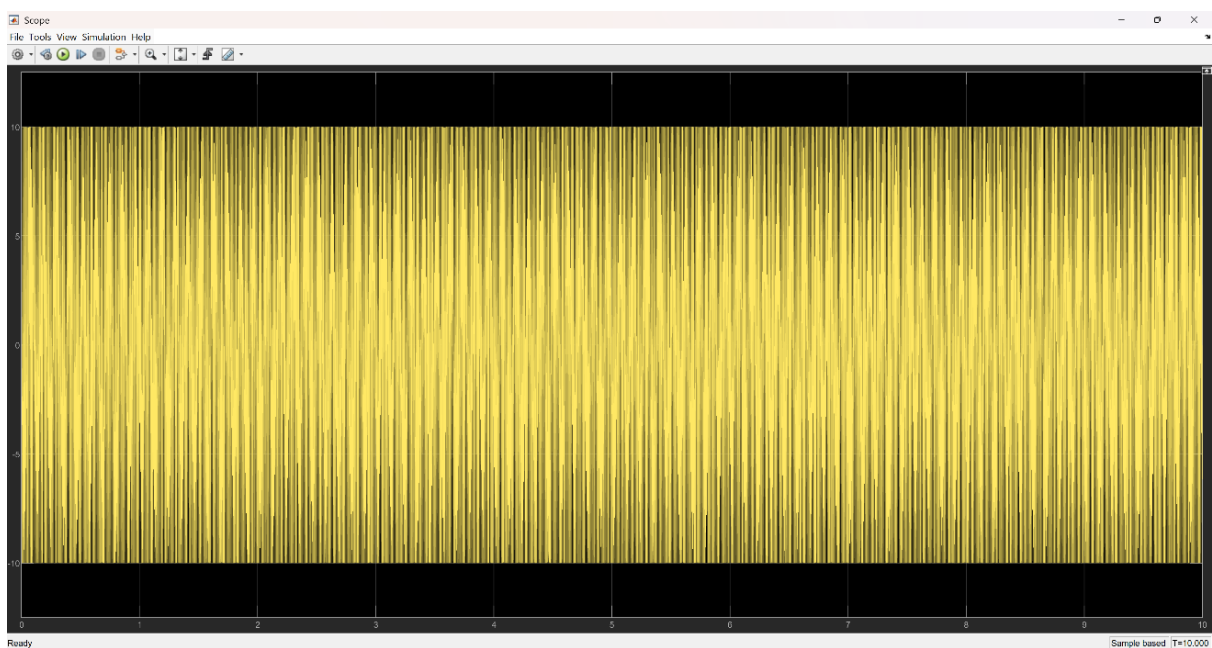Step 2: Once we run the model, by putting in different values for AC Voltage Frequency, we get the following results: (i) Peak Voltage [10 V]



(ii) Final results:

